


(Boolean Algebra)

→ Step - 30 for electronic circuit

- Base of variable ($r = 2$)

variables - (A, B, C, \dots, Z) or (a, b, e, \dots, z) .

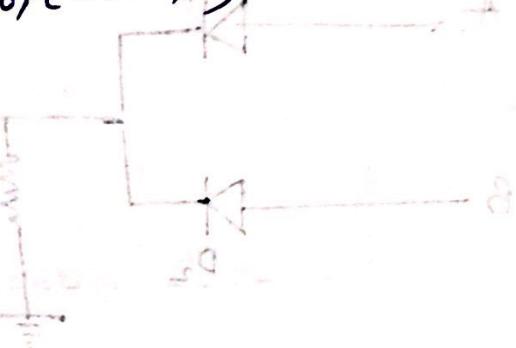operators - $\underbrace{\text{OR, AND}}_{\text{binary}}, \underbrace{\text{NOT}}_{\text{unary}}$



(i) OR - $\{+, \cup, \vee\}$

(S) ~~Notation~~ ~~for~~ ~~distilling~~ ~~the~~ ~~terms~~ ~~that~~ ~~are~~


$y = A+B$ or $A \cup B$ or $A \vee B$ $y = A+B+C$
(2-variables) (3-variables)

A	B	$y = A+B$
0	0	0
0	1	1
1	0	1
1	1	1
0	0	0
0	1	1
1	0	1
1	1	1


A	B	C	y
0	0	0	$0 + 0 = 0$
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

$(y \text{ only } 1^0 \text{ when all I/P's are } 0)$

OR-gate

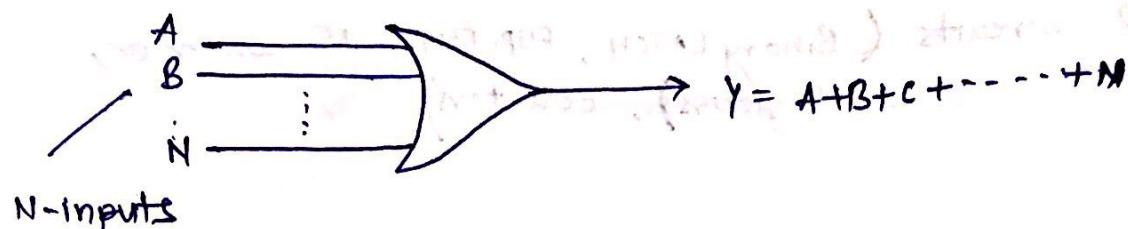

Internal circuits of OR-gate:-

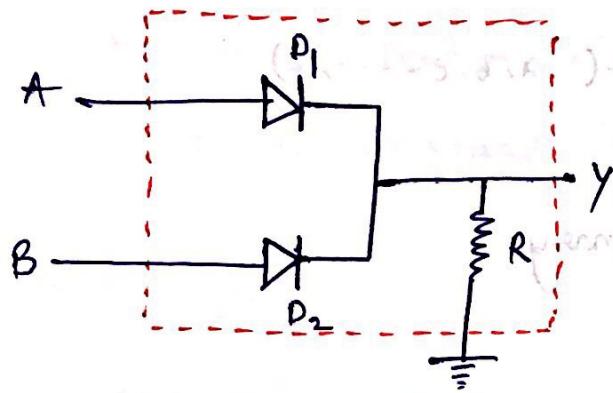

- Truth Table consist all possible 2^n combination (2^n) for n-inputs with corresponding output-

(i) AND opⁿ: {., ∩, ∧}

$$Y = A \cdot B$$


A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

$$Y = A \cdot B \cdot C$$

A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

(Y is 1 when all I/P are 1 otherwise 0)





AND - gate :

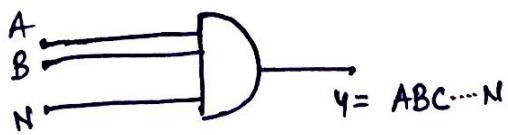

NOTE:- for $Y = A \cdot f(A, B)$	
OR	AND
if $A=0$	$Y=B$
$A=1$	$Y=1$
$B=0$	$Y=A$
$B=1$	$Y=1$
	$Y=A$

NOTE:- Enable I/P which allows other I/P's to pass the value.

Disable I/P which blocks other I/P's.

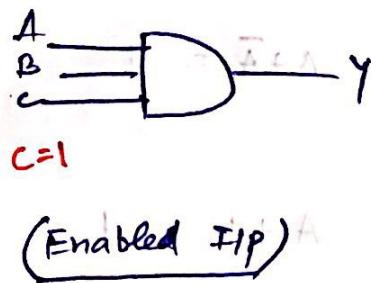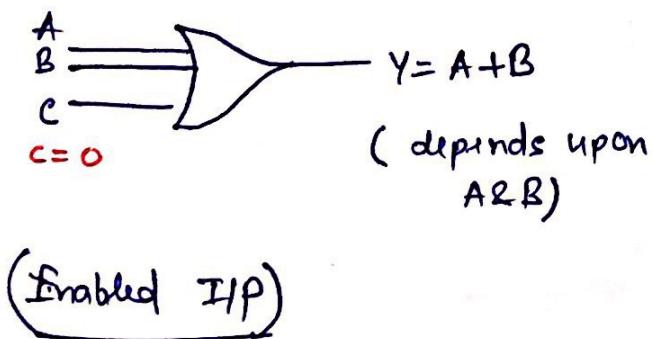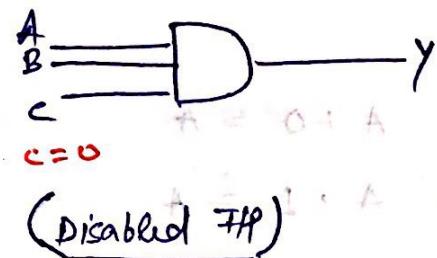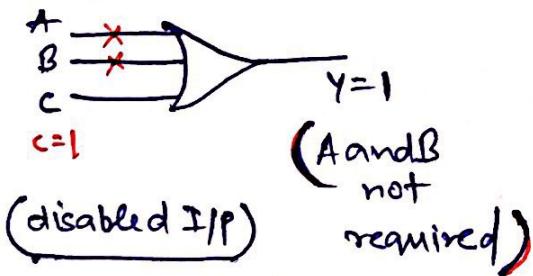

(iii)

NOT : { - , 1 }

$$Y = \bar{A} \text{ or } A'$$

A	Y
0	1
1	0


$$0 = v \quad 1 = v \quad 0 = 0 \quad 1 = 1$$

NOT gate

$$P = v \quad J = Y \quad S = 0$$



Truth table + CUA

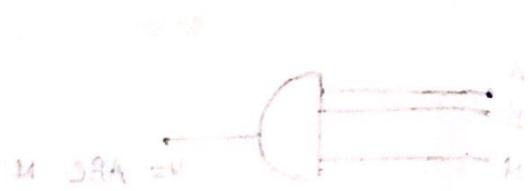

Boolean algebra Properties:-

1. $A + A + A + \dots + A = A$

2. $A \cdot A \cdot A \cdot \dots \cdot A = A$

3. $A + 0 = A$

$A \cdot 1 = A$

3. $A \cdot \bar{A} = 0$

4. $A + \bar{A} = 1$

5. $A + 1 = 1$

6. $A \cdot 0 = 0$



Identity

(Commutative property)



Identity

(Associative property)



(Identity property)

5: Principal of Duality
[OR \leftrightarrow AND
0 \leftrightarrow 1]

Q: find the dual of given boolean expression:

$$\bar{A} + B [C + \bar{D} (E + \bar{F})]$$

$$\text{Dual} \rightarrow \bar{A} [B + C (\bar{D} + E\bar{F})]$$

NOTE:

variable ' x ' \Rightarrow contains specific x or \bar{x}

literal ' x ' \Rightarrow can contain both x or \bar{x}
form,

6: $(\bar{A}) = A$

7: $A + BC = (A+B)(A+C)$ $\xrightarrow{\text{distributive property}}$
 $A(B+C) = (A \cdot B) + (A \cdot C)$ $\xleftarrow{\text{dual}}$

8: $A + \bar{A}B = A + B$

9: $\bar{A} + AB = \bar{A} + B$

10: $A + AB = A(1+B) = A$

Q. Identify minimum no. of logic gates to realize given expression:

$$\bar{x}\bar{y}z + [xz + yz]$$

(a) 0

(b) 1

(c) 2

(d) None

$$[(\bar{x} + \bar{y})z + z] \bar{A} \leftarrow \text{logic}$$

$$\bar{x}\bar{y}z + xz + yz$$

$$\bar{x}\bar{y}z + (xz + yz)z \Leftrightarrow (\bar{x}\bar{y} + (x+y))z$$

$$(x + \bar{y} + y)z$$

$$(x + 1)z = z$$

no logic gate required

$$A = \bar{(\bar{A})}$$

Q. simplified form of given boolean expression:

$$AB + \bar{A}B + A\bar{B}$$

$$\text{Ans} \rightarrow (B \cdot A) + (\bar{B} \cdot A) = (B + \bar{B})A$$

(a) A

(b) $A + \bar{B}$

(c) $A + B$

(d) None

$$B + A = B\bar{A} + A$$

$$= (A + \bar{A})B + A\bar{B}$$

$$= B + A\bar{B}$$

$$= (B + A)(B + \bar{B})$$

$$= (B + A)$$

$$B + \bar{A} = BA + \bar{A}$$

$$BA + A$$

Q: $\underline{AB} + ABC + \underline{A}\bar{B}C\bar{D}$

- (a) $\bar{A}(B+c)$ (b) $A(\bar{B}+c)$ (c) $B(\bar{A}+\bar{c})$ (d) None

$$= \bar{A}\bar{B} + ABC$$

$$= A(\bar{B} + BC)$$

$$= A(\bar{B} + c)$$

II: $\underline{AB} + \underline{\bar{AC}} + \underline{BC} = A\underline{B} + \bar{A}\underline{C}$

redundant

[Consensus property
or
Redundant property]

$$= AB + \bar{A}C + BC \cdot 1$$

$$= AB + \bar{A}C + BC(A + \bar{A})$$

$$= \underline{AB} + \bar{A}C + \underline{ABC} + \bar{A}BC$$

$$= AB + \bar{A}C + \bar{A}CB$$

$$= \underline{(AB + \bar{A}C)}$$

$$(A+B) \cdot (\bar{A}+c) \cdot (B+c) = (A+B) \cdot (\bar{A}+c)$$

redundant

12: $\overline{(A+B+C)} = \bar{A} \cdot \bar{B} \cdot \bar{C}$

$$\overline{(AB \cdot C)} = \bar{A} + \bar{B} + \bar{C}$$

[De-morgan's property]

Q. Apply De-morgan's Law —

$$\bar{A} + B \left(C + \overline{D(E+F)} \right)$$

$$A (\bar{B} + \bar{C} (D + \overline{E \cdot F}))$$

$$\bar{B}A + \bar{C}A =$$

$$(\bar{B} + \bar{C})A =$$

$$(D + \bar{E})A =$$

Q. If $f(A, B) = \bar{A} + B$ then

$$F(F(x+y, y), z) = ?$$

(a) $\bar{x}y + z$

(b) $x\bar{y} + z$

(c) $y + \bar{x}z$

(d) None

$$= \overline{(\bar{x}+y + y)} + z$$

$$= \overline{(\bar{x}+y)} + y + z$$

$$= ((x+y) \cdot \bar{y}) + z$$

$$= (x\bar{y} + 0) + z$$

$$= \underline{\underline{x\bar{y} + z}}$$

$$(\bar{A}+A)\bar{B} + \bar{B}\bar{A} + \bar{B}A =$$

$$\bar{B}\bar{A} + \bar{B}A + \bar{B}A =$$

$$\bar{B}(\bar{A} + A) =$$

$$(0+1)(1+0) = 1$$

Therefore,

$$\bar{B} \cdot \bar{B} \cdot \bar{A} = \overline{(B+B+A)}$$

$$\bar{B} + \bar{B} + \bar{A} = \overline{(B+B+A)}$$

Q. If $\underline{\bar{x} * y} = \bar{x} + y$ and $z = x * y$ then

$$z * x = ?$$

(a) y

(b) \bar{x}

(c) \bar{x}

(d) None

$$= (\cancel{\bar{x} * y}) * x$$

$\begin{array}{c} \cancel{\bar{x}} \\ \cancel{*} \\ \cancel{y} \end{array} + \begin{array}{c} \cancel{\bar{x}} \\ \cancel{*} \\ \cancel{y} \end{array} \end{array} + x$
$$= (\bar{x} + y) * x$$

$$\bar{z} * x = \bar{z} + yx$$

$$= \overline{(x * y)} + yx$$

$$= \overline{(x + y)} + yx$$

$$= (x \cdot \bar{y}) + yx$$

$$[(\bar{x} + y + z) \cdot \bar{x}] \cdot \bar{x} = \bar{x}$$

Q. $v + \bar{v}\omega + \nabla\bar{\omega}x + \bar{v}\bar{w}\bar{x}y + \bar{v}\bar{w}\bar{x}\bar{y}z$

$$\bar{v}\bar{w}\bar{x}(\underbrace{y + \bar{y}z})$$

$$\bar{v}\bar{w}x + \bar{v}\bar{w}\bar{x}(y + z)$$

$$\bar{v}w + \bar{v}\bar{w}(x + y + z)$$

$$= v + \bar{v}(w + x + y + z)$$

$$= \underline{(v + w + x + y + z)}$$

$$Q: \overline{AB} + \overline{BC} + \overline{CA} + \underline{\overline{BC}} + B + \underline{\overline{C}}$$

$$\overline{CA} + \overline{C} + B$$

$$\overline{AB} + \overline{BC} + \overline{C} + B$$

$$\overbrace{\underline{B} + \overline{B}C + \overline{C}} \\ \ast (B + C) + \overline{C}$$

$$B + 1$$

$$\overline{A} + \overline{B} = 1 \quad \textcircled{1}$$

$$\overline{B} + \overline{C} = 1$$

$$\overline{B} + \overline{(C + B)} =$$

$$Q: (\overline{AC}) + \overline{BC} [AC + D(\overline{B} + \overline{ACD})]$$

$$= \overline{AC} + \overline{BC} [\overline{AC} (\overline{D} + \underline{B + \overline{ACD}})]$$

$$= \overline{AC} + \overline{BC} (\cancel{\overline{AC} \cdot \overline{D}} + \cancel{\overline{AC} \cdot B} + \overline{AC})$$

Q: Find the values of Boolean variable A, B, C & D

while solving the following Boolean eq:

$$\overline{A} + AB = 0$$

$$(A + \overline{A} + B + \overline{B}) V + W = V$$

$$\overline{AB} = AC$$

$$(A + \overline{A} + B + \overline{B} + C + \overline{C}) V + W = V$$

$$AB + BC + CA = CD$$

$$\overline{A+B} = 0 \quad A=1 \quad B=0 \quad C=1 \quad D=0$$

$$AB = AC \quad \text{at } A=1 \text{ & } B=0 \Rightarrow 0+0+1 = \underline{\underline{1 \cdot D}}$$

$$\overline{B} = \underline{\underline{C}}$$

$$\overline{A+B} \in D$$

$$\boxed{\begin{array}{l} A=1 \\ B=0 \\ C=1 \\ D=0 \end{array}}$$

- 1 is 0 & 0 is 1 which is derived in different way

$$\overline{D} \in \overline{D} = \underline{\underline{0}}$$

$$D \in D = \underline{\underline{1}}$$

f(x,y,z) = $\bar{x}y + y\bar{z} + x\bar{y}z$ - Sum-of-Product form
(OR)

f(x,y,z) = $(\bar{A}+B)(\bar{B}+C)(A+\bar{B}+C)$ - Product-of-sum form
(AND)

~~The truth table of~~

Q: The truth table of $f(A,B,C)$ is given below -

A	B	C	$f(A,B,C)$
0	0	0	0
1	0	1	1
2	0	0	1
3	0	1	1
4	1	0	1
5	1	0	0
6	1	0	1
7	1	1	0

SOP :-

- Refer to only those combination of truth table where the function output is 1

- if the variable is having value as 0 or 1 -

$$\begin{cases} x=0 \Rightarrow \bar{x} \\ x=1 \Rightarrow x \end{cases}$$

- Then OR all the combination.

$$\begin{aligned}
 \text{SOP} &= f_1 + f_2 + f_3 + f_4 + f_6 \\
 &= (\bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C} + ABC) \\
 &\quad \text{min-terms} \\
 &\quad \text{canonical SOP form}
 \end{aligned}$$

Minterm - It is a product term, it contains all the variable either (complementary or un-complementary), and the corresponding function output must be 1.

$$\begin{aligned}
 f(A, B, C) &= \sum(m_1, m_2, m_4, m_6) \\
 &= \sum(1, 2, 4, 6)
 \end{aligned}$$

POS :-

- Refer to those combination of truth table where the function output is 0.

- if $m=0 \rightarrow x$

$$x=1 \Rightarrow \bar{x} \quad \text{in Maxterm}$$

- Apply AND opⁿ on maxterms


$$POS = (A+B+C) (\bar{A}+\bar{B}+\bar{C}) (\bar{A}+B+\bar{C}) (\bar{A}+\bar{B}+\bar{C})$$

$$= \overline{\pi(0,3,5,7)}$$

canonical POS form

$$= (A+B+C) (\bar{A}+B+\bar{C}) (\bar{B}+\bar{C})$$

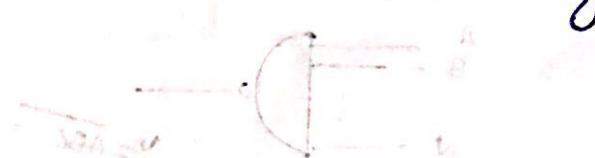Maxterm - It is a sum term, it contains all the variables either (x or \bar{x} form), where the corresponding function output is 0.



feedback

String Sec

Derived operators :-

(i) NAND - AND \rightarrow NOT \overline{AB}

$$Y = \overline{AB}$$

$$Y = \overline{ABC \dots}$$


A	B	$Y = \overline{AB}$
0	0	1
0	1	1
1	0	1
1	1	0

A	B	C	X	Y
0	0	0		1
0	0	1		1
0	1	0		1
0	1	1		1
1	0	0		1
1	0	1		1
1	1	0		1
1	1	1		0

The result of NAND opⁿ is 0 if and only all the variables are 1.

NAND gate :

De-morgan's law

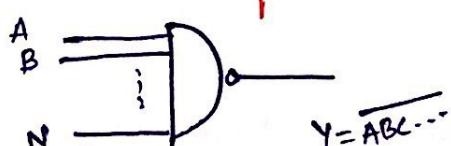

Bubbled
- OR gate

if $A=0$ then $y=1$ ← disabled I/P $A=0$

$A=1$ then $y=\overline{B}$ ← enabled I/P $A=1$

(ii) NOR - OR → NOT $\overline{A+B}$



		<u>enable I/P</u>	<u>disable I/P</u>	<u>Y</u>
<u>A</u>	<u>B</u>			
0	0	0	1	1
0	1	0	1	0
1	0	0	1	0
1	1	0	1	0

<u>A</u>	<u>B</u>	<u>C</u>	<u>Y</u>
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

The O/p of NOR gate is zero if at least one of the variable is 1.

NOR gate:-

De-morgan's law

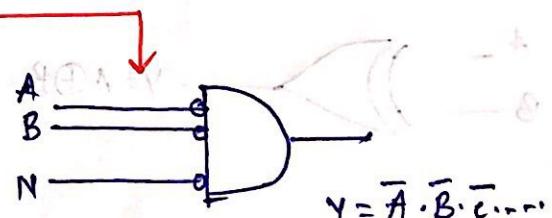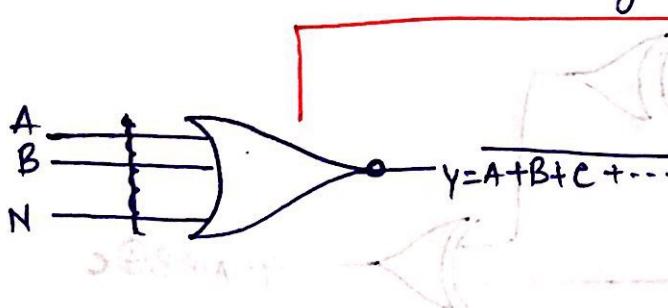

if $A=1$ then $y=0$ ← disabled I/P

$A=0$ then $y=\overline{B}$ ← enabled I/P

(iii) EX-OR (exclusive - OR)

$$Y = A \oplus B \\ = \bar{A}B + A\bar{B}$$



$$Y = \bar{A} \oplus B \oplus C$$


A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0
0	0	0
0	1	1
1	0	1
1	1	0
0	0	0
0	1	1
1	0	1
1	1	0

A	B	C	Y
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

The o/p is 1 whenever odd number of variables are 1 hence it is named as ODD function.

XOR gate

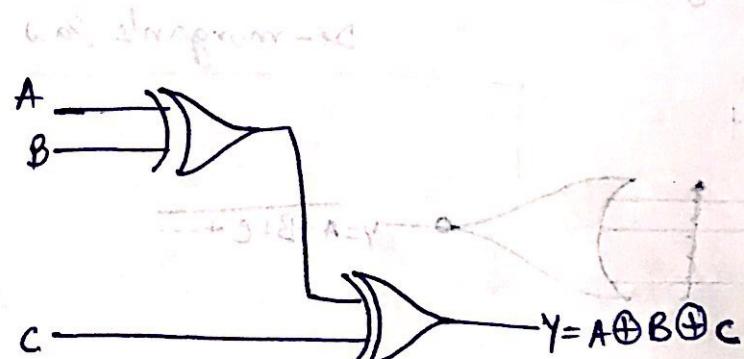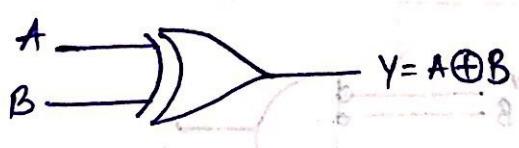

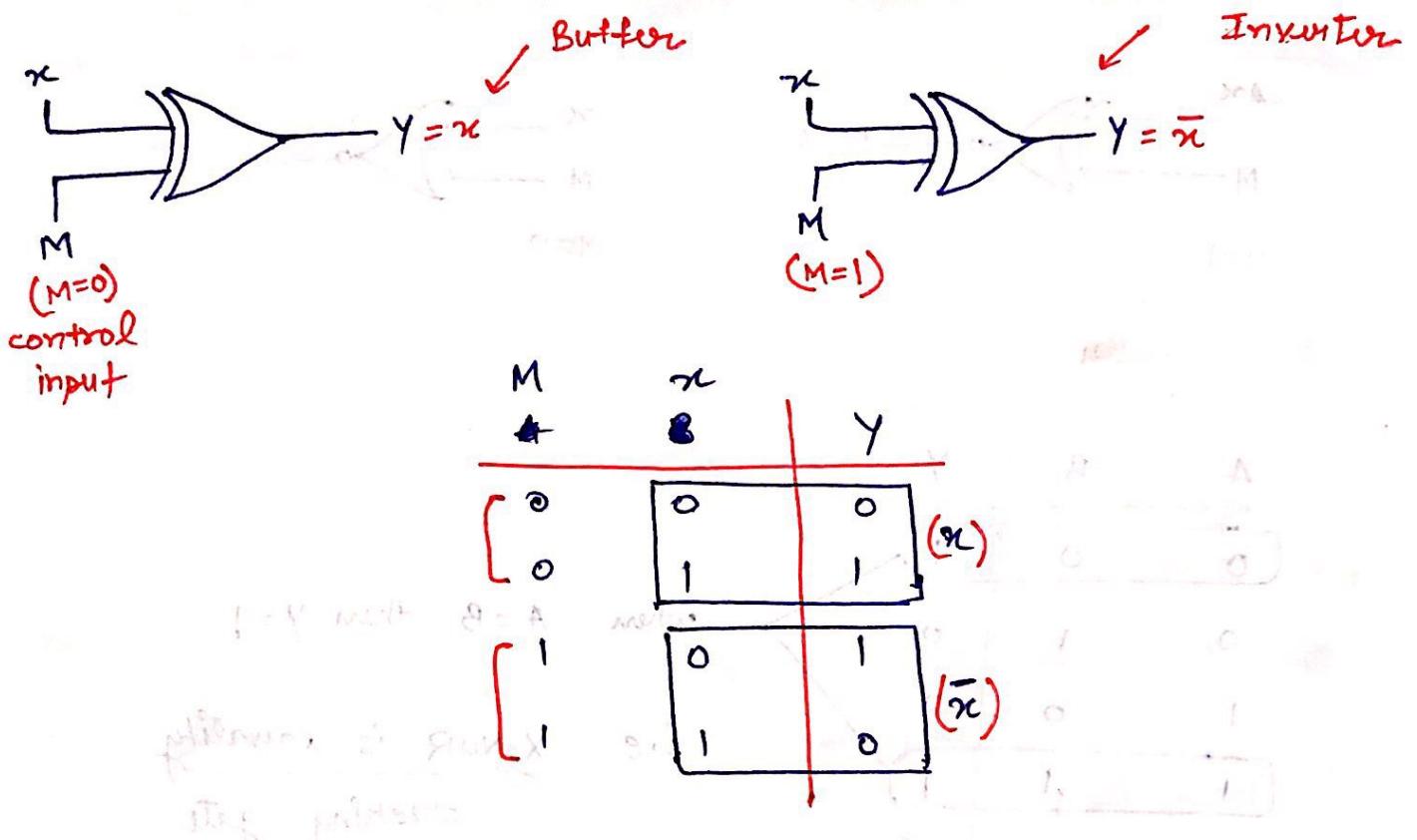

NOTE: There we can't assign any input as enabled or disabled

(iv) Ex - NOR (Only defined on two variables or I/p)

$$y = A \oplus B \text{ or } \overline{A \oplus B} \quad (\text{Ex-OR} \rightarrow \text{NOT})$$




A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1

$$\begin{aligned}
 y &= A \oplus B \\
 &= \overline{AB} + AB \quad \text{SOP} \\
 &= (A + \overline{B})(\overline{A} + B) \quad \text{POS}
 \end{aligned}$$

$$S(000) + S(001) =$$

$$S(010) + S(011) =$$

$$S(100) + S(101) =$$

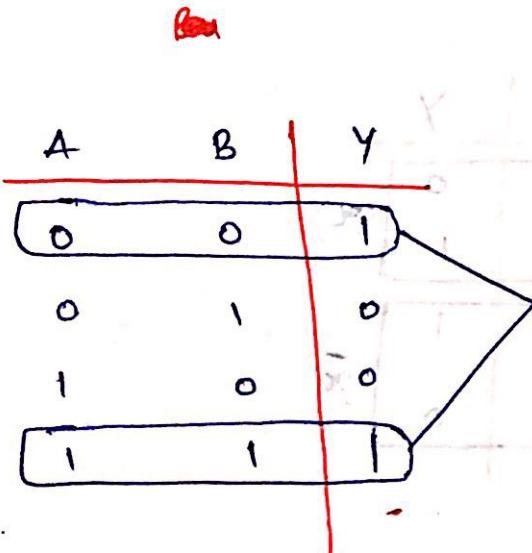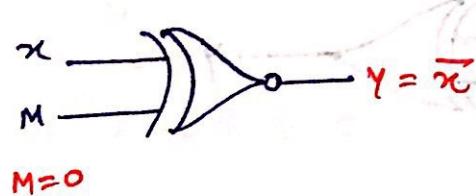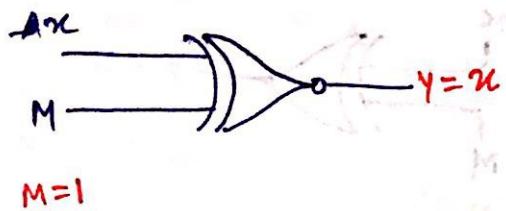

when $A=B$ then $Y=1$

i.e. X-NOR is equality checking gate

Identical to below in logic gate after this we start

NOTE:- whatever gate we build (for) \oplus \ominus \otimes \odot

\oplus - inequality checking gate

\ominus - inequality checking gate

Q. why more than 2 - inputs are allowed

is \oplus \ominus .

$$Y = \frac{A \odot B \odot C}{M}$$

$$= M C + \overline{M} \overline{C}$$

$$= (A \oplus B) C + (A \oplus B) \overline{C}$$

$$= (\overline{A \oplus B}) C + \frac{(A \oplus B) \overline{C}}{M} = \overline{M} C + M \overline{C}$$

$$= \underline{A \oplus B \oplus C}$$

Thus ~~XOR~~ converts to XOR for odd number of inputs.

NOTE :- For odd number of inputs XOR and XNOR behaves same.

NOTE :- Associativity are valid on OR, AND, & EX-OR, and not valid on NOR & NAND

Q. Simplify given Boolean expressions:

i) $(A \oplus B) \oplus (A \oplus \bar{B})$ \perp

ii) $A \oplus A\bar{B} \oplus \bar{A}$ $\bar{A} + B$

iii) $(A \oplus A) \oplus (B \oplus \bar{B})$ associativity

$(A \oplus A) \oplus \perp$

$0 \oplus \perp$ (\perp)


iv) $A \oplus A\bar{B} \oplus \bar{A}$

$A \oplus \bar{A} \oplus A\bar{B}$ associativity

$\perp \oplus A\bar{B}$

$0 \cdot A\bar{B} + \perp (\bar{A} + B) = (\bar{A} + B)$

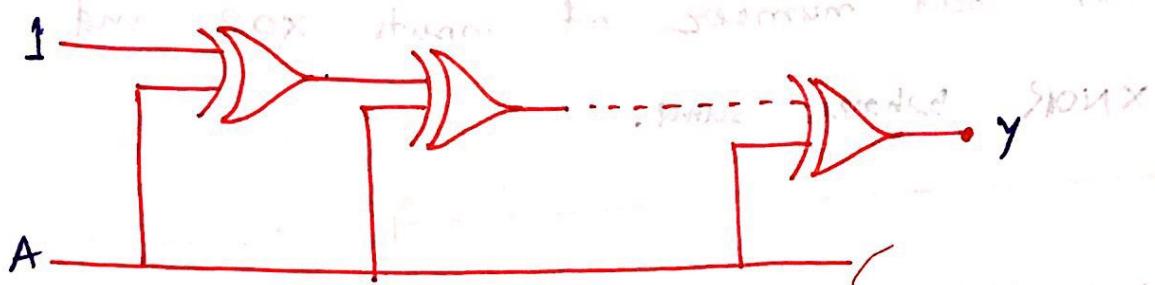Q. In a given ckt 20 XOR gates are cascaded as shown below. The output by each -



(a) A

(b) \overline{A}

(c) \downarrow

(d) 0

$$= 1 \oplus A \oplus A \oplus \dots \oplus A$$

$$= 1 \oplus 0$$

$$= 1$$

Q. In the given Boolean express A is having

XOR opⁿ n - no. of times 1 if ~~missed~~ $(A \oplus A) \oplus (A \oplus A)$

(i). n is odd

• 0

$1 \oplus (A \oplus A)$

(ii). n is even

• A

$$Y = A \oplus A \oplus \dots$$

when n is ^{even} ~~odd~~ $n = 2$

$$Y = \underbrace{A \oplus A \oplus A}_{0} = A$$


if n is even ($n=4$)

$$Y = \underbrace{A \oplus A}_{0} \oplus \underbrace{A \oplus A}_{A} \quad (0)$$

Q: $Y = A \oplus A \oplus A \oplus \dots$, A is repeating
 n - number of times.

so, for n even $Y = 0 = (A \oplus A)$
 n odd $Y = A = (A \oplus A \oplus A)$

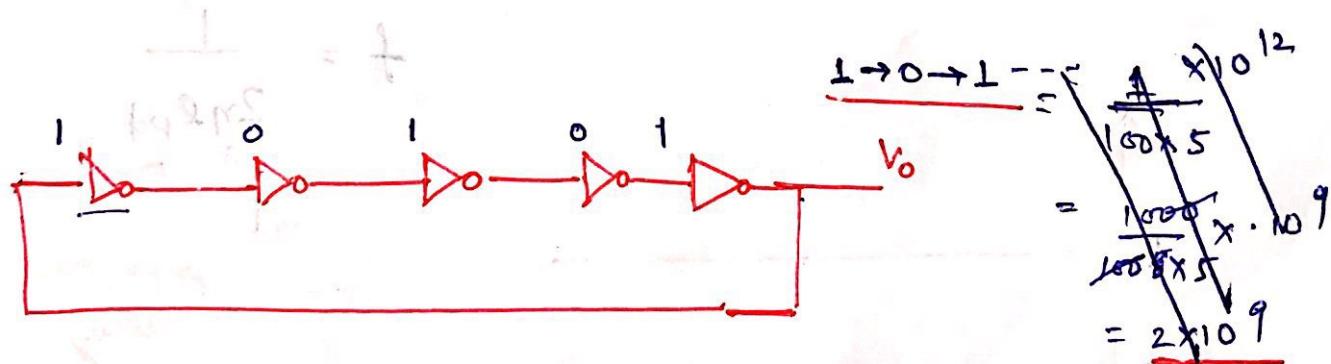Q: In the given ckt each not gate has propagation delay of 100ps, what is the frequency of output signal V_o -



(a) 500 kHz

(b) 1 GHz


(c) 2 GHz

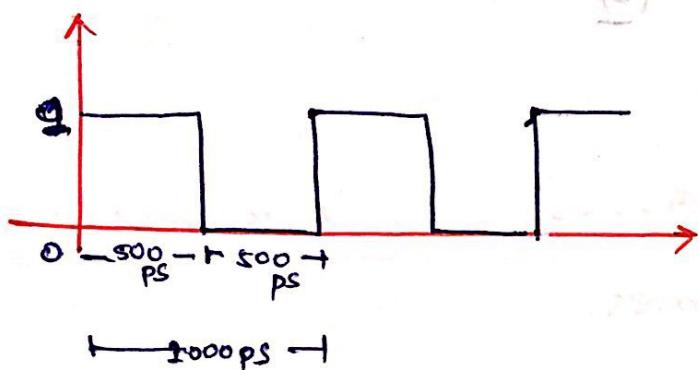(d) None




12

The propagation delay is the amount of time taken by the logic gate to respond for the given input.



$$\text{so, } f = \frac{10^{12}}{1000} = 10^9 \text{ Hz} = 1 \text{ GHz}$$

Q:

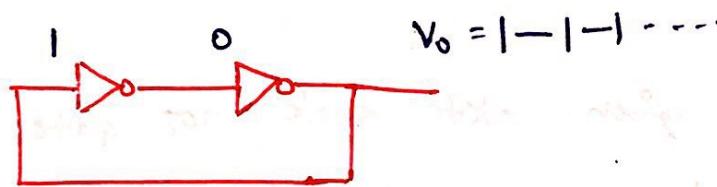

no change in waveform -

$$f = \frac{1}{2\eta L_{pd}}$$

odd
propagation delay

