

## EX-OR & EX-NOR properties:-

1.  $A \oplus A = 0$

2.  $A \odot A = 1$

3.  $A \oplus 0 = A$

4.  $A \odot 0 = \bar{A}$

5.  $A \oplus 1 = \bar{A}$

6.  $A \odot 1 = A$

7.  $A \oplus \bar{A} = 1$

8.  $A \odot \bar{A} = 0$

9.  $\bar{A} \oplus \bar{B} = A \oplus B$

10.  $\bar{A} \odot \bar{B} = A \odot B$

11. if  $A \oplus B = C$

then  $A \oplus C = B$

$B \oplus C = A$

$A \oplus B \oplus C = 0$

12. if  $A \odot B = C$

then  $A \odot C = B$

$B \odot C = A$

$A \odot B \odot C = 1$

Let  $x = \bar{A}$ ,  $\bar{x} = A$

$y = \bar{B}$ ,  $\bar{y} = B$

$\bar{A} \oplus \bar{B} = x \oplus y$

$= x\bar{y} + \bar{x}y$

$= \underline{A \oplus B}$

13. if  $A \oplus B \oplus C = A \oplus D$

then  $A \oplus B \oplus D = C$

$A \oplus C \oplus D = B$

$B \oplus C \oplus D = A$

$A \oplus B = C \oplus D$

$A \oplus C = B \oplus D$


$B \oplus C = A \oplus D$

$A \oplus B \oplus C \oplus D = 0$


\* NAND & NOR are functionally complete set universal logic gates.

Using NAND :-


NOT

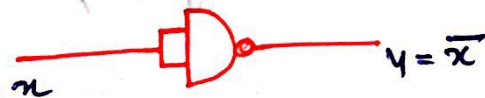

AND

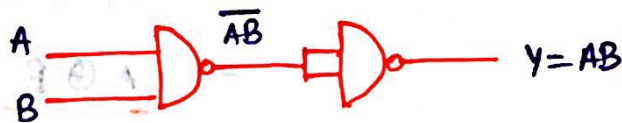


OR

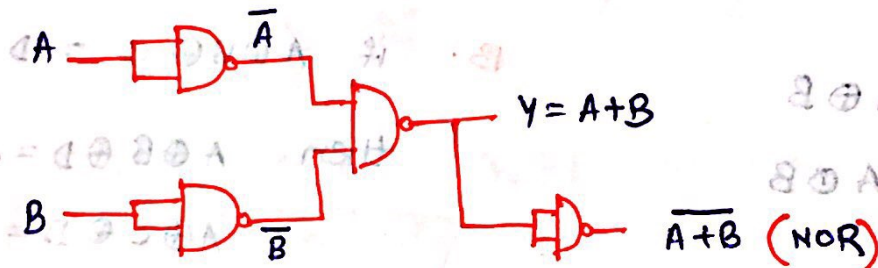


Using NOR :-


NOT

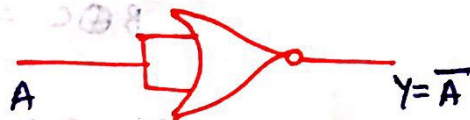


OR  
AND

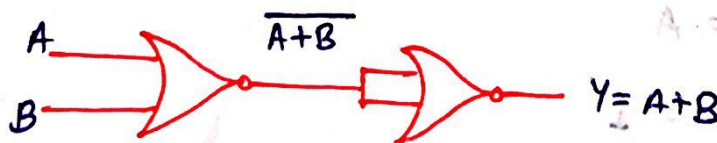

AND

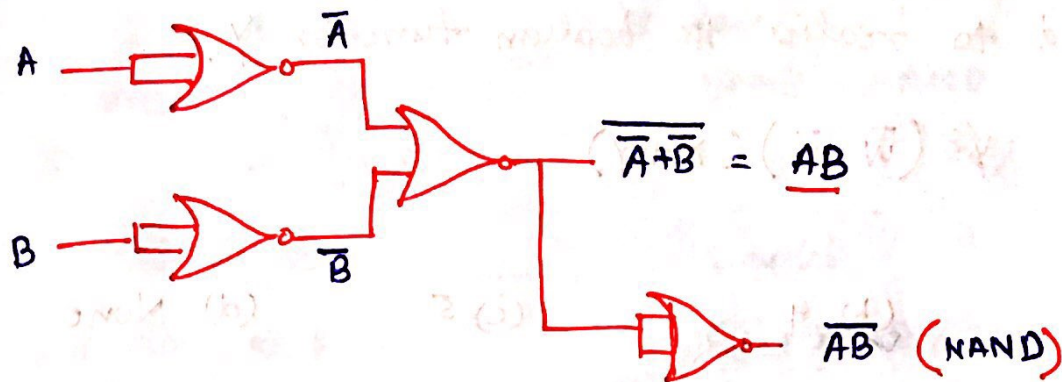

NOTE:-

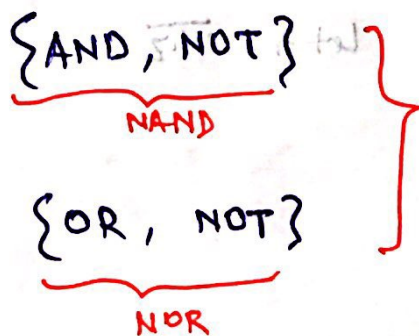


Functionally complete

Q. Identify the minimum no. of 2 I/p NAND Gates requires to realize the boolean function.

$$f(A, B, C) = A\bar{B}C$$

- (a) 3 (b) 4 (c) ☒ 5 (d) 6

$$f = (AC)\bar{B}$$

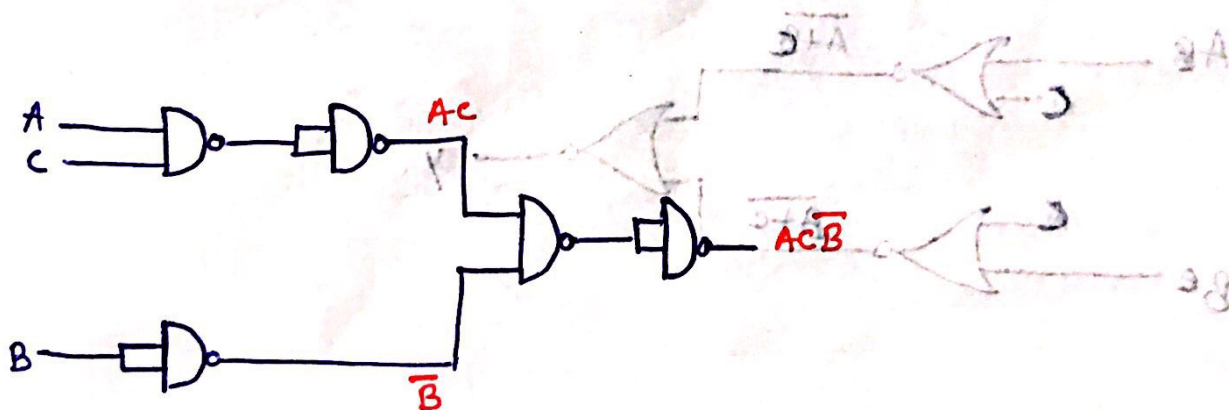



Q. Identify the minimum no. of 2 I/p NAND gates required to realize the boolean function  $Y$ .

$$Y = (\bar{W} + \bar{Z})(X + Y)$$

- (a) 3      (b) 4      (c) 5      (d) None


$$Y = \overline{W \cdot Z} (X + Y)$$

$$Y = A(X + Y)$$

$$Y = AX + AY$$

$$Y = \overline{AX \cdot AY}$$

$$A = \overline{W \cdot Z}$$

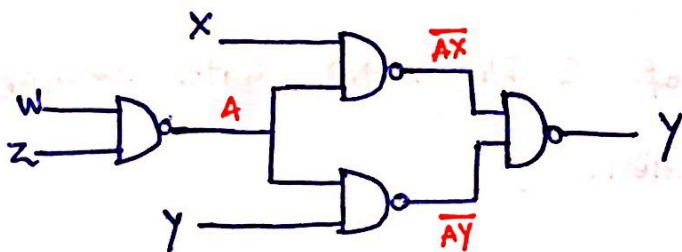


Q. Identify minimum no. of 2 I/p NOR gates required to realize the boolean function  $Y = C + AB$ .

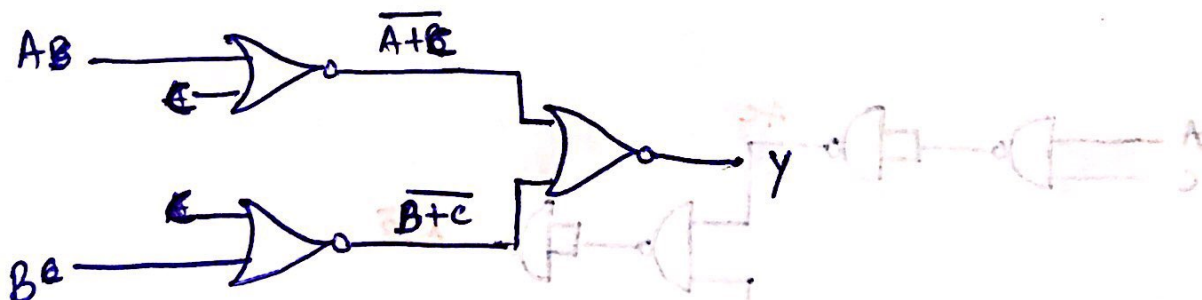- (a) 3      (b) 4      (c) 5      (d) None.

$$Y = (C + A)(C + B)$$

$$Y = \overline{\overline{A+C} + \overline{B+C}}$$



NOTE : -

2 level  
AND - OR



2 level  
NAND - NAND

2-level  
OR - AND




2 level  
NOR - NOR

$$(\bar{B} + \bar{A})(B + A) =$$

$$(\bar{B} + \bar{A}) \bar{B} A =$$

$$f(x, y, z)$$

Q:

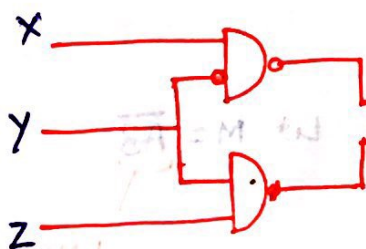


What is the minimum no. of NAND & NOR gates to implement the above ckt.

(a) 1, 4

(b) 4, 1

(c) 2, 4

(d) None

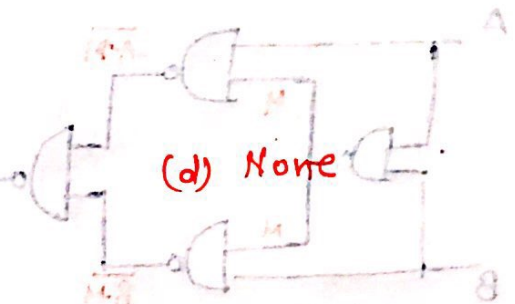

$$f = \overline{(\bar{x}\bar{y} \cdot yz)} = \overline{\bar{x}\bar{y}} + \overline{yz}$$

$$= (\bar{x} + \bar{y}) + yz$$

$$= \overline{\bar{x}yz + yz}$$

$$= \overline{yz}$$

1 NAND

4 NOR

Q. Minimum no. of two I/p NAND gates required to realize XOR gate.

- (a) 3    (b) 4    (c) 5    (d) None

$$Y = A \oplus B$$

$$= A \oplus B$$

$$= (A+B)(\bar{A}+\bar{B})$$

$$= \bar{A}\bar{B}(A+B)$$


$$= M(A+B)$$

$$= \underline{MA + MB}$$

3 NAND

$$\text{Let } M = \bar{A}\bar{B}$$

1 NAND

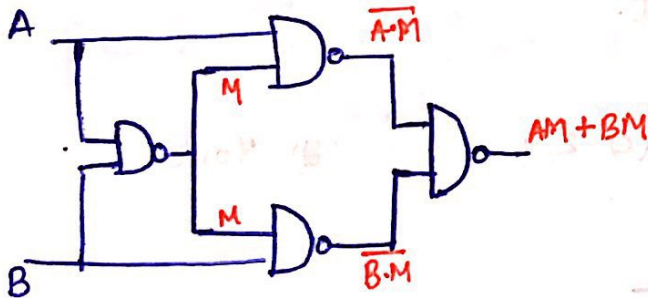

Q. Minimum no. of two I/p NAND gates required to realize XNOR gate

- (a) 3    (b) 4    (c) 5    (d) None




Q. Identity min. no. NOR gate required to realize 2-I/P X-NOR gate.

- (a) 3      ~~(b) 4~~      (c) 5      (d) None

$$\begin{aligned}
 Y &= A \odot B \\
 &= \bar{A}\bar{B} + AB \\
 &= \frac{A+B}{M} + AB \\
 &= (M+A)(M+B)
 \end{aligned}$$

1 NOR → M  
3 NOR → (M+A)(M+B)

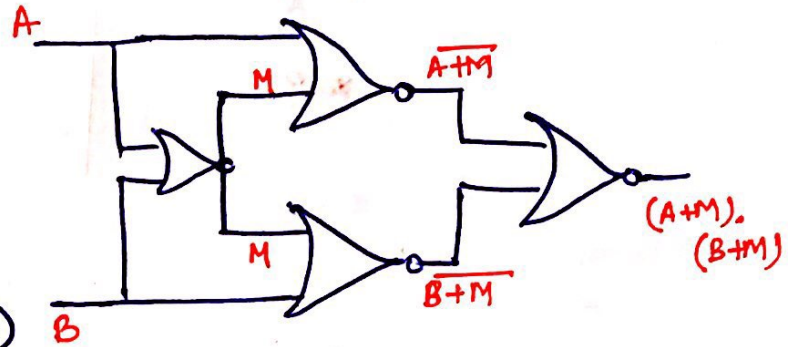

	2 I/P NAND	2 I/P NOR
NOT	1	1
AND	2	3
OR	3	2
NOR	4	—
XOR	4	5
XNOR	5	4
NAND	—	4

Gate	Alternate gate
NAND	Bubbled OR
NOR	Bubbled AND
NAND	Bubbled NOR
NOR	Bubbled NAND



	NAND (2n-2)	NOR (3n-3)
$f_1 = AB$	2	3
$f_2 = ABC$	4	6
$f_3 = ABCDE$	8	12
$f_4 = A\bar{B}$	3 ( <u>2+1</u> )	2 ( <u>3-1</u> )
$f_5 = A\bar{B}\bar{C}D\bar{E}$	8 ( <u>10-2</u> )	10 ( <u>12-2</u> )

} complimen  
exception



	NAND (3n-3)	NOR (2n-2)
$f_1 = A+B$	3	2
$f_2 = A+B+C$	6	4
$f_3 = A+B+C$ $+D+E$	12	8
$f_4 = A+B$	$2(3-1)$	$3(2+1)$
$f_5 = A+B+C$ $+D+E$	$10(12-2)$	$10(8+2)$

complement exception

Q. Identify whether the given boolean is a self dual function.

$$f(x, y, z) = \sum m(1, 2, 4, 7)$$

consider for the function  $f$ ,  $f_d$  is the dual function. if  $(f_d = f)$  then function  $f$  is said to be self dual function.

$$f_d = \bar{x}\bar{y}z + \bar{x}y\bar{z} + x\bar{y}\bar{z} + xyz$$

$$f_d = (\bar{x} + \bar{y} + z) \cdot (\bar{x} + y + \bar{z}) \cdot (x + \bar{y} + \bar{z}) + (x + y + z)$$

$$= \pi(0, 3, 5, 6)$$

$$= \sum(1, 2, 4, 7)$$

$$\text{so, } \boxed{f_d = f}$$

Q. How many self dual functions are possible using 3 boolean variables.

(a) 8

✓ (b) 16

(c) 32

(d) None

Total no. of minterm =  $2^n = 2^3 = 8$

so, there must be • exact  $2^{n/2} = 8/2 = \underline{4 \text{ terms}}$

in a function to be a self dual.

Mutally exclusive pairs for self dual

0  $\longleftrightarrow$  7

1  $\longleftrightarrow$  6

2  $\longleftrightarrow$  5

3  $\longleftrightarrow$  4

(0, 7), (1, 6), (2, 5), (3, 4)

choose 1  
from each  
pair

so, we have total  $2^{n/2} = \underline{2^{n-1}} \text{ pairs} = m$

out of these pairs

only 1 can be selected

so, we have 2 choices  
for each pairs

Total no. of  
function  
possible

=

2

where m is total  
pair possible

$(= (2)^{2^{n-1}})$

n is no. of  
boolean variable

NOTE :- Natural function is the func<sup>n</sup> which has equal no. of minterms and maxterms.

For function to be a self dual function, it must be a natural function.