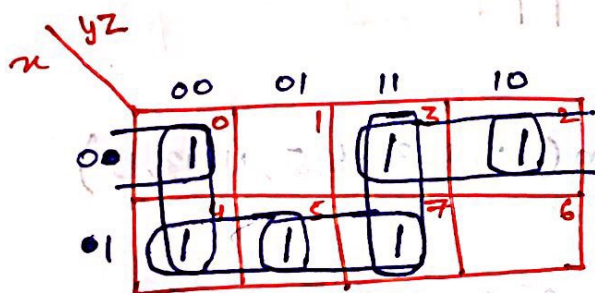


Reading minimal form :-

- Cover all the minterm with minimum number of subcubes and each subcube must be as big as possible.

Q: Identify the number of prime implicants, Essential PI and write all possible minimal expression.

$$f(x, y, z) = \sum m(0, 2, 3, 4, 5, 7)$$



$$PI = 6$$

$$EPI = 0$$

Prime implicants -

$$h_1 = \bar{y}\bar{z} (0, 4)$$

$$h_2 = x\bar{y} (4, 5)$$

$$h_3 = xz (5, 7)$$

$$h_4 = yz (3, 7)$$

$$h_5 = \bar{x}y (2, 3)$$

$$h_6 = \bar{x}\bar{z} (0, 2)$$


Minimal expression :-

$$f = \bar{y}\bar{z} + xz + \bar{x}y$$

$$f = \bar{x}\bar{z} + x\bar{y} + yz$$

* Every minterm is covered by 2 prime implicants and hence thus corresponding K-map is called as cyclic PI K-map.

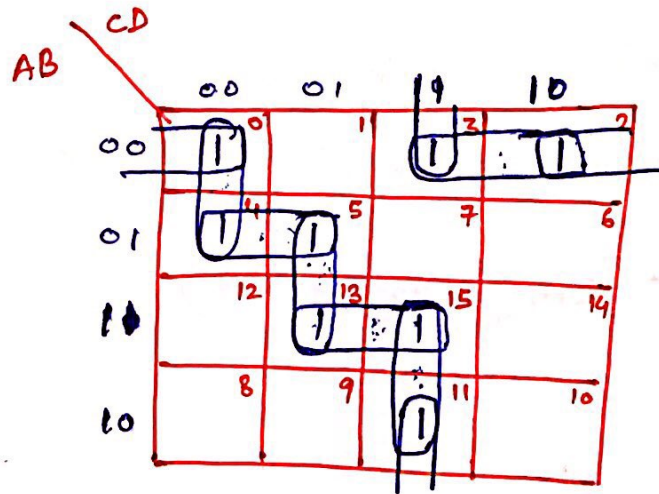Q: Develop a 4-variable funcⁿ with 8 minterms and the K-map must be cyclic PI K-map. For the above funcⁿ identify the number of PI, EPI, and all possible minimal expression.



$$PI = 8$$

$$EPI = 0$$

$$f(A, B, C, D) = \sum m(0, 2, 3, 4, 5, 11, 13, 15)$$

$$f_1 = \bar{A}\bar{C}\bar{D} + \bar{B}\bar{C}D + A\bar{C}\bar{D} + \bar{A}\bar{B}C$$

$$f_2 = \bar{A}\bar{B}\bar{C} + ABD + \bar{B}CD + \bar{A}\bar{B}\bar{D}$$

NOTE:-

→ If the funcⁿ is having cyclic PI K-map;

- no. of PI = no. of minterms

- no. of EPI = 0


- Each PI is having $(n-1)$ no. of literals in its product form where n is no. of variables in the given function.

- Functⁿ has having 2 minimal forms.

- no. of terms in minimal expression = half of no. of PI

- There is no common PI among two minimal expression.

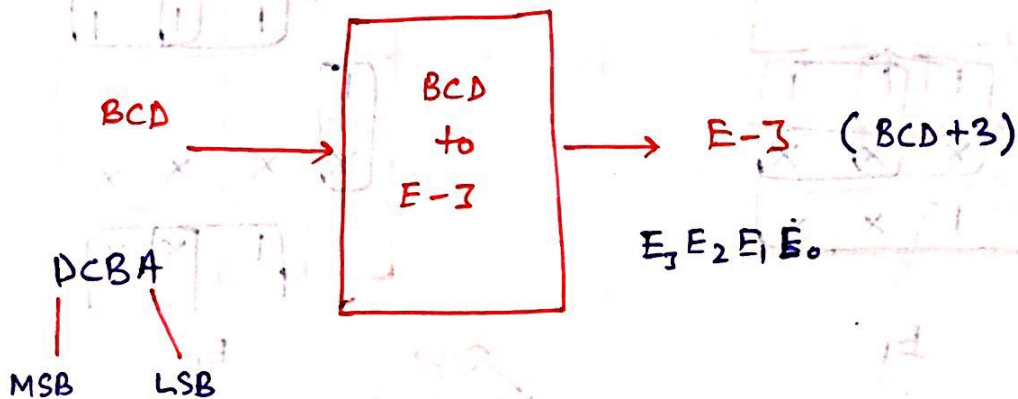Q. Design and realize BCD to excess-3 code converter.



$$\begin{aligned} \text{BCD} &= \{0, 1, 2, \dots, 9\} \\ \text{E-3} &= \{3, 4, 5, \dots, 12\} \end{aligned}$$

Truth Table:-





	D	C	B	A	E ₃	E ₂	E ₁	E ₀
0	0	0	0	0	0	0	1	1
1	0	0	0	1	0	0	1	0
2	0	0	1	0	0	1	0	0
3	0	0	1	1	0	1	1	0
4	0	1	0	0	0	1	0	0
5	0	1	0	1	1	0	0	0
6	0	1	1	0	1	0	1	0
7	0	1	1	1	1	0	1	1
8	1	0	0	0	1	0	1	1
9	1	0	0	1	1	1	0	0

$$E_3(D, C, B, A) = \sum m(5, 6, 7, 8, 9) + d$$

$$E_2(D, C, B, A) = \sum m(1, 2, 3, 4, 9) + d$$

$$E_1(D, C, B, A) = \sum m(0, 3, 4, 7, 8) + d$$
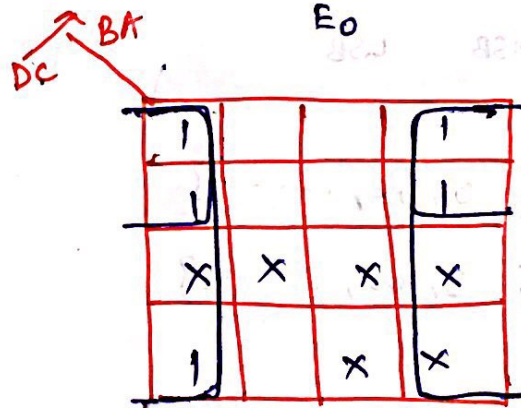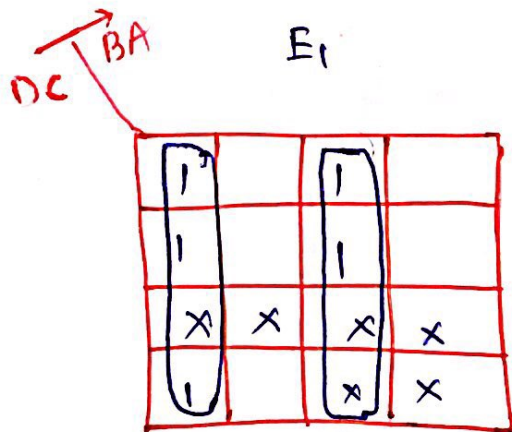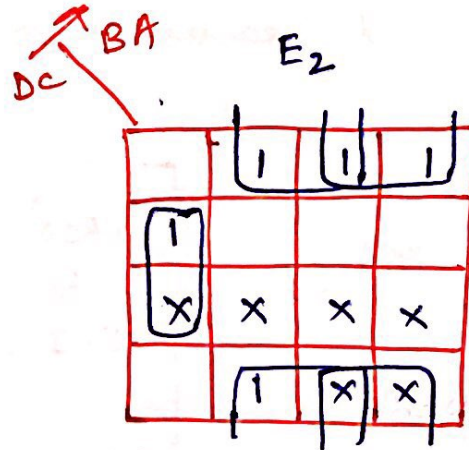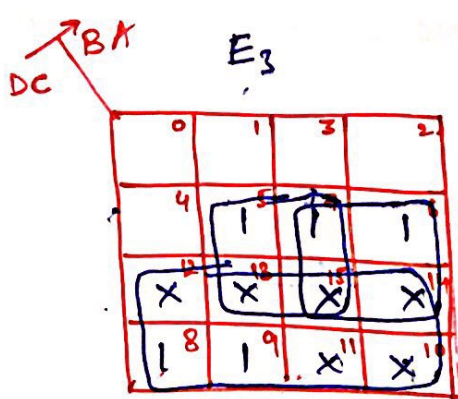
$$E_0(D, C, B, A) = \sum m(0, 2, 4, 6, 8) + d$$



(i) In some digital ckt, few of I/p combination may not be used by ckt.

OR

(ii) Few I/p combination ckt may not be responding

OR

(iii) For few I/p combination o/p may be simply ignored

The above combination are called 'Don't care' combination.

As in case of BCD (0, 1, 2, ..., 9) where $n=4$ we have

$2^4 = 16$ combination, but (10, 11, 12, ..., 15) combination are not used so there are don't care combination.

$$(d = \sum m(10, 11, 12, 13, 14, 15))$$

To cover the minterms while using "don't care" combinations if the size of the subcube is coming large, such don't care are included in the subcube.

$$E_3 = D + CA + CB$$


$$E_2 = C\bar{B}\bar{A} + \bar{C}A + \bar{C}B$$

$$E_1 = \bar{B}\bar{A} + BA = A \oplus B$$

$$E_0 = \bar{A}$$

Logic designing

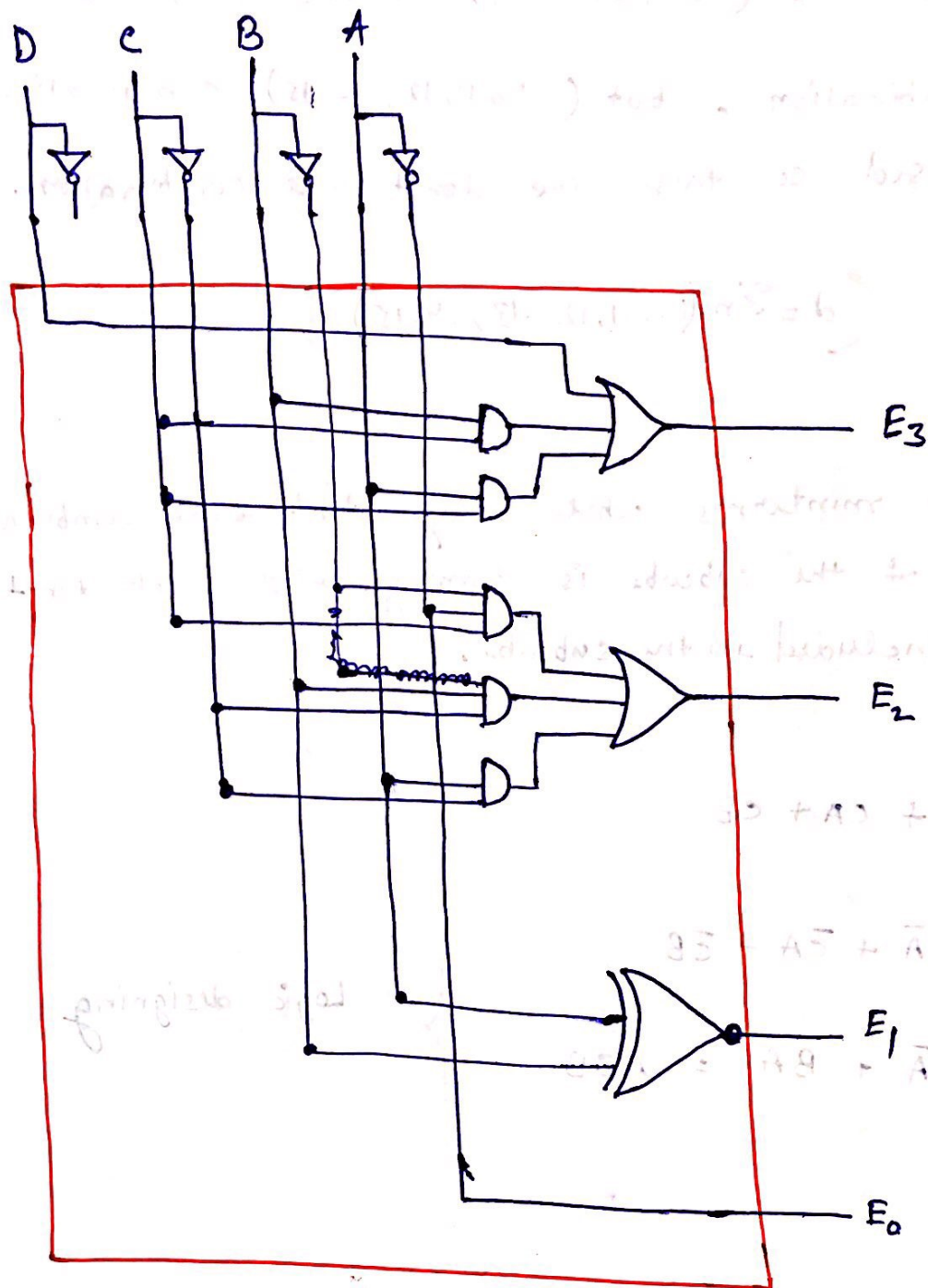The process of analyzing truth table to generate logic function is ~~nothing~~ known as gate designing.



Steps to Design 1-ckt:-

- (i) Read the Truth table
- (ii) Generate canonical sop form using truth table.
- (iii) Read minimal forms using K-maps.
- (iv) Develop the logic 1-ckt for minimal expression.

Advantage:-

- (i) No. of logic gates is minimum.
- (ii) Fan-in for logic gate is minimum.
- (iii) Power consumption is less
- (iv) Complexity of the ckt is less
- (v) Cost of ckt is less.

Q. The funcⁿ f_1 and f_2 are given below:

$$f_1(w, x, y, z) = \sum m(1, 4, 5, 9, 12, 14, 15) + d(3, 10)$$

$$f_2(w, x, y, z) = \sum m(0, 2, 3, 5, 11, 12, 15) + d(6, 14)$$

(a) Find $f_3 = f_1 + f_2$

(b) $f_4 = f_1 \cdot f_2$

(c) $f_5 = f_1 \cdot \overline{f_2}$

m	f_1	f_2	$\overline{f_2}$	$f_3 = f_1 + f_2$	$f_4 = f_1 \cdot f_2$	$f_5 = f_1 \cdot \overline{f_2}$
0	0	1	0	1	0	0
1	1	0	1	1	0	1
2	0	1	0	1	0	0
3	X	1	0	1	X	0
4	1	0	1	1	0	1
5	1	1	0	1	1	0
6	0	X	X	X	0	0
7	0	0	1	0	0	0
8	0	0	1	0	0	0
9	1	0	1	1	0	1
10	X	0	1	X	0	X
11	0	1	0	1	0	0


m	f_1	f_2	f_2'	f_3	f_4	f_5
12	ϕ	1	0	1	ϕ	0
13	0	0	1	0	0	0
14	1	X	X	1	X	X
15	1	1	0	1	1	0

$$f_3 = \sum m(0, 1, 2, 3, 4, 5, 9, 11, 12, 14, 15) + d(6, 10)$$

$$f_4 = \sum m(5, 12, 15) + d(3, 14)$$

$$f_5 = \sum m(1, 4, 9) + d(10, 14)$$

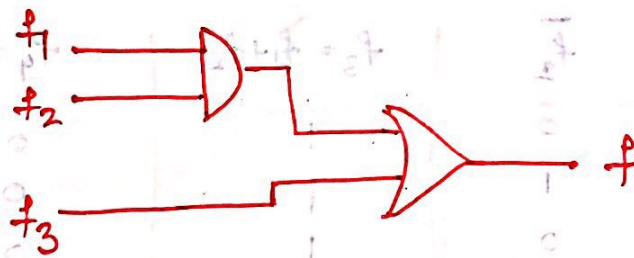Q: The given logic ckt realizing the funcⁿ $f(w, x, y, z)$
 $= \sum m(1, 4, 7, 9, 10, 12, 15)$ and funcⁿ $f_1(w, x, y, z)$
 $= w\bar{y} + x\bar{y}z + \bar{w}\bar{x}y$. Find f_2 and f_3 .



$$f_1(w, x, y, z) = w\bar{y} + x\bar{y}z + \bar{w}\bar{x}y$$

$$= \cancel{w\bar{y} + x\bar{y}z + \bar{w}\bar{x}y}$$

$$= w\bar{x}\bar{y} + w\bar{x}y + w\bar{x}y\bar{z} + \bar{w}\bar{x}y\bar{z} + \bar{w}\bar{x}yz + \bar{w}\bar{x}y\bar{z}$$

$$f_1 = \overset{13}{\omega \pi \bar{y} z} + \overset{12}{\omega \pi \bar{y} \bar{z}} + \overset{9}{\omega \pi \bar{y} z} + \overset{8}{\omega \pi \bar{y} \bar{z}} + \overset{5}{\bar{\omega} \pi \bar{y} z} + \overset{3}{\bar{\omega} \pi \bar{y} z} + \overset{2}{\bar{\omega} \pi \bar{y} \bar{z}}$$

$$f_1 = \sum m(2, 3, 8, 9, 10, 12, 13)$$

$$f = f_1 \cdot f_2 + f_3$$


	f_1	f_2	f_3	f
0	0	X	0	0
1	0	X	1	1
2	1	0	0	0
3	1	0	0	0
4	0	X	1	1
5	1	0	0	0
6	0	X	0	0
7	0	X	1	1
8	1	0	0	0
9	1	1	X	1
10	0	X	1	1
11	0	X	0	0
12	1	1	X	1
13	1	0	0	0
14	0	X	0	0
15	0	X	1	1

$$f_2 = \sum m(9, 12) + d(0, 1, 4, 6, 7, 10, 11, 14, 15)$$

$$f_3 = \sum m(1, 4, 7, 10, 15) + d(9, 12)$$

Minterms of the f_2 are don't care of f_3

Q:

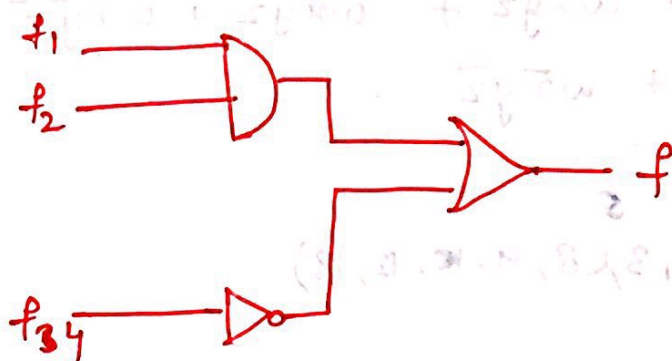

Find f_2 and f_4 , $f = \sum m(1, 4, 7, 9, 10, 12, 15)$

$$f_1 = \sum m(2, 3, 5, 8, 9, 12, 13)$$

$$f_4 = \overline{f_3} = \sum m(0, 2, 3, 5, 6, 8, 11, 13, 14) + d(9, 12)$$

Q: Find the minimal POS form for the funcⁿ f :


$$f(A, B, C, D) = \pi M(1, 5, 7, 10, 12, 13, 15)$$

AB \ CD	00	01	11	10
00		0	1	
01		0	0	0
11	0	0	0	
10				0

$$f = (\overline{B} + \overline{D}) \cdot (\overline{A}\overline{B} + \overline{B} + C) \cdot (\overline{A} + B + C) \cdot (\overline{A} + B + \overline{C} + D)$$

SOP \rightarrow Product term \rightarrow Prime Implicant

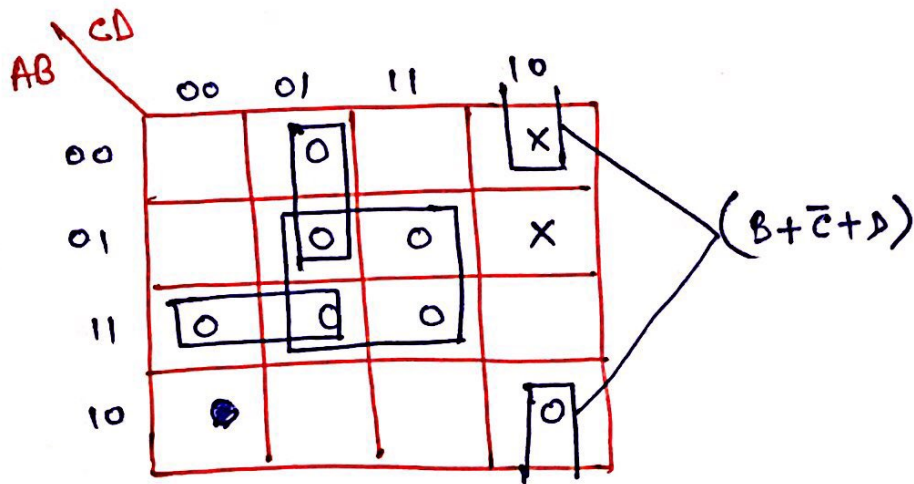POS \rightarrow Sum term \rightarrow False Prime Implicant



Q. Identify the number of minterms in the given function:

$$f(v, w, x, y, z) = y + xz$$

(a) 24

(b) 20

(c) 16

(d) 12

